

**Lab Final Exam (Circuits Portion)**  
**COMP 122/L**  
**Fall 2017**

**Score breakdown:**

Assembly (online): 35  
Arithmetic Logic Unit: 33  
Register File: 32  
Total: 100

Please write your name below, and **wait until told to begin:**

Once told to begin, tear out the last sheet of this document, which contains the questions to answer. You can use this to easily refer back to the question while you answer it.

**Ground Rules**

1. You may have three 8 1/2 x 11 inch sheets of paper in front of you containing handwritten notes covering both sides of each sheet. It does not need to be the same sheet from last week.
2. If you have a question, raise your hand and I will come to you.
3. You **may not** communicate with anyone else. **Violations of this rule will result in a 0 on the exam.** This exam is purely individual effort.



## **Arithmetic Logic Units**

Write your solution below.

**Register Files**

Write your solution below.

## Arithmetic Logic Units

Design a 3-bit ALU which supports subtraction and bitwise AND. This ALU takes the following inputs:


Input Name	Input Description
A0	Bit 0 of the first operand
A1	Bit 1 of the first operand
A2	Bit 2 of the first operand
B0	Bit 0 of the second operand
B1	Bit 1 of the second operand
B2	Bit 2 of the second operand
Op	The operation to perform; 0 for subtraction and 1 for AND

Given the above inputs, the ALU produces the following outputs:

Output Name	Output Description
U0	Bit 0 of the result
U1	Bit 1 of the result
U2	Bit 2 of the result
Cout	Carry-out for subtraction. This output is permitted to take on any value you want if the input operation isn't subtraction.
V	Overflow for subtraction. This output is permitted to take on any value you want if the input operation isn't subtraction.

For this task, you may use **only** the following components, in unlimited supply:

 - AND, OR, and NOT gates
- 2-input multiplexers
- Single-bit adders, shown to the right. Given two single-bit inputs A and B, along with a single carry-in bit Cin, this produces a single-bit result R and a carry-out bit Cout



## Register Files

Design a register file holding two 3-bit registers. The register file takes the following inputs:

Input Name	Input Description
WE	Short for “Write Enable”; set to 1 if we are writing to a register, else 0
CLK	The system clock
R	Which register we are reading from / writing to; 0 for the first register and 1 for the second register
I0	Bit 0 of the input to write. Ignored if WE = 0.
I1	Bit 1 of the input to write. Ignored if WE = 0.
I2	Bit 2 of the input to write. Ignored if WE = 0.

Given the above inputs, the register file produces the following outputs:

Output Name	Output Description
U0	Bit 0 of the result
U1	Bit 1 of the result
U2	Bit 2 of the result

For this task, you may use **only** the following components, in unlimited supply:

- AND, OR, and NOT gates
- 2-input multiplexers
- D flip-flops